Final Exam

Due online Thursday, June 14 at 10:30 PM

Because this is the final exam for the course, I need to see your own work.


No collaboration with other students is allowed.

You may use your notes, books, and online references to answer the 2 problems.

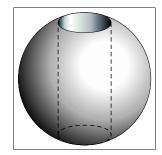1. Solid Body Calculations

A sphere of radius R and uniform density ρ has a cylindrical hole of radius r drilled through its exact center. For the purposes of this problem, we can assume $\rho = 1 \, \text{kg/m}^3$, $R = 0.5 \, \text{m}$, and $r = 0.3 \, \text{m}$.


Use Monte Carlo integration to calculate the inertial properties of this object.



- (a) Calculate the total mass of the object.
- (b) Calculate the moment of inertia about the shared axis of symmetry (call it \hat{z}).
- (c) Calculate the moment of inertia about the " \hat{x} axis" (any axis orthogonal to \hat{z}).

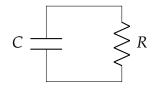2. RC Circuit Behavior

The "RC circuit" is composed of a resistor *R* and capacitor *C* in a series circuit driven by a voltage or current source.



The circuit behavior is given by the equation

$$R\frac{dq}{dt} + \frac{1}{C}q = U(t),$$

where q is the capacitor charge, dq/dt = I is the circuit current, and U(t) is the applied voltage.

We would like to know how the system responds to a square input voltage pulse:

$$U(t) = \begin{cases} 0, & t < t_1 \\ U_0 = 6 \, \text{V}, & t_1 \le t \le t_2 \\ 0, & t > t_2 \end{cases}$$

In this problem, we will assume $R = 100 \Omega$, $C = 4.7 \times 10^{-5} \,\mathrm{A} \,\mathrm{s} \,\mathrm{V}^{-1}$ *.

- (a) Assuming q(0) = 0, solve the differential equation numerically and plot q(t) and I(t) over the interval $0 < t < t_{\text{final}}$, with $t_1 = 0$, $t_2 = 2RC$, and $t_{\text{final}} = 4RC$.
- (b) Compare your result for the current to the analytic solution

$$\bar{I}(t) = \frac{U_0}{R} \left(e^{-(t-t_1)/RC} \Theta(t-t_1) - e^{-(t-t_2)/RC} \Theta(t-t_2) \right),$$

where $\Theta(x)$ is the Heaviside step function.

^{*}This unit is almost exactly the same as the Farad, but not exactly!